

[Report #MP3 – the music codec]

GROUP #1

HUGO BASTIN

LOÏC TUMELAIRE

VINCENT DIEUZEIDE

ZÉPHYRIN BARRAS

Analog filter: selection and sizing

Provide the schematics of the filter

Sallen and key second order filter where we suppose $R=R1=R2=R3, C=C1=C2$


Provide the values of the components

We first choose $R1=100k\Omega$ because the cut-off frequency desired is 40 hz with $f_c=1/2\pi RC$ so we need a large R to have an acceptable $C=39.79nF$, despite the bigger thermal noise this Large value of resistance will induce.


The we choose the value of R4 with the following formula

$$K = 1 + \frac{R4}{R3} \quad Q = \frac{1}{3 - K}$$

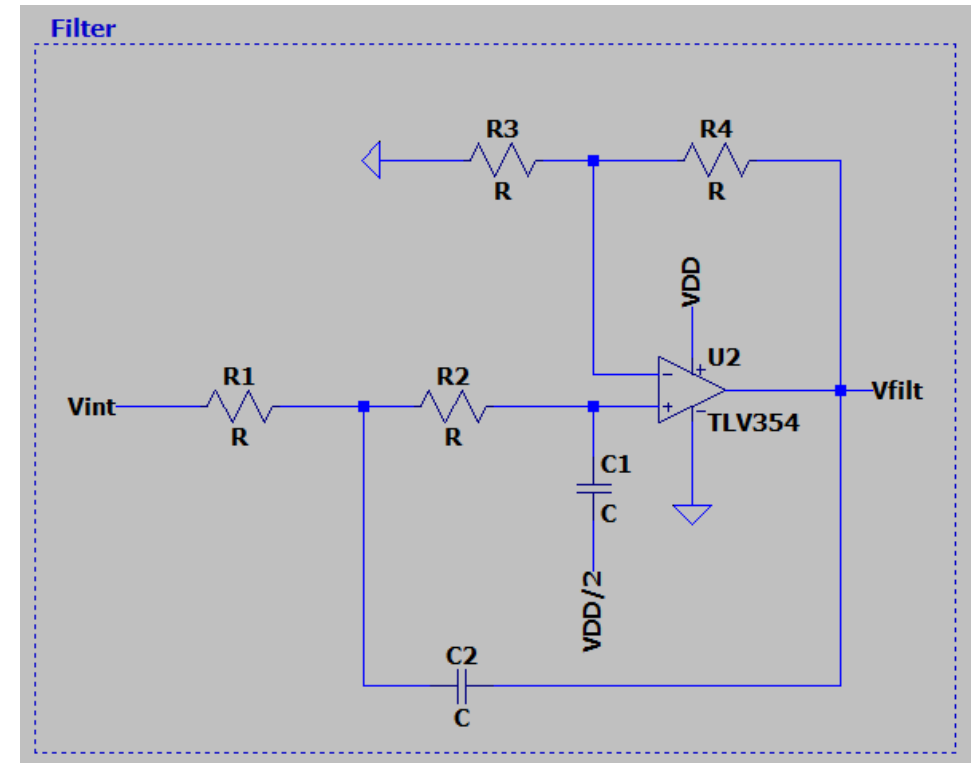
We found, for $Q=0.707$ (to avoid overshoot response) , $R4=58k\Omega$



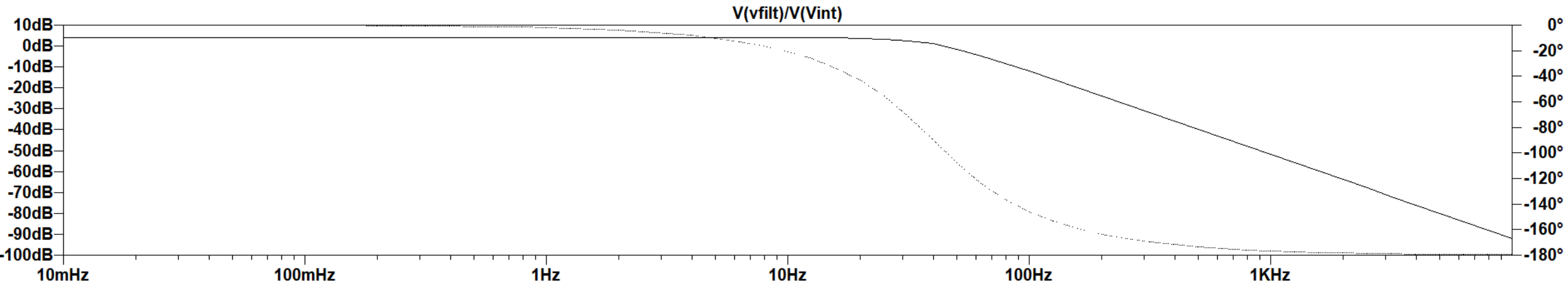Simulate the filter frequency response using LTSpice:



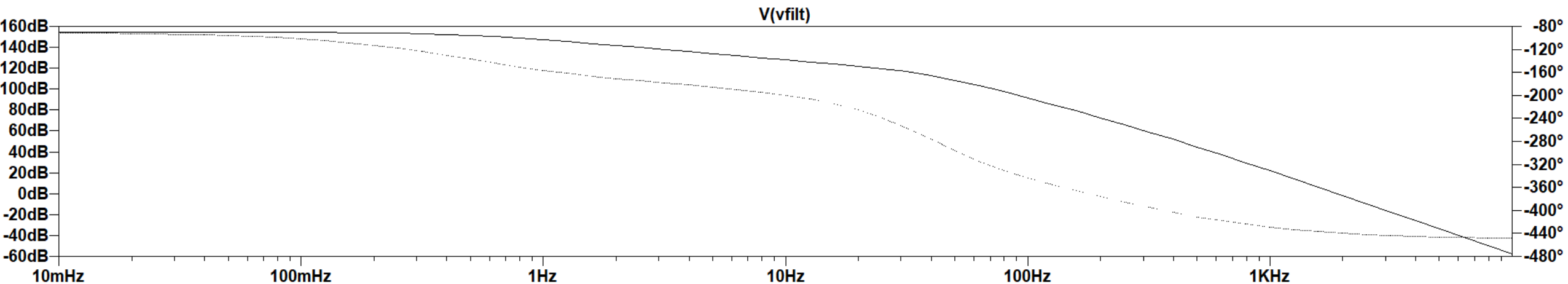Simulate the whole instrumentation chain using LTSpice:



Whole chain noise analysis (1/2)

- Evaluate the impact of each noise source on the performance of the whole chain.
- Use the final expression of the noise analysis document Part 1 for the charge amplifier block.
 - Consider only the noise of the TLV354 for the filter block (do not account for noise coming from the resistors).

Bring back the noise reference of the enter of the filter for the output noise filter (only TLV354 noise considered)

Voltage:

From datasheet: **Low Noise:** $7.5 \text{ nV}/\sqrt{\text{Hz}}$, with a band from 0.5 to 40 Hz.

Gain is 4dB. We find $\text{voltage_noise_input_filter}=187 \text{ nV}$

Current:

From datasheet:

i_n	Current noise density	$f = 1 \text{ MHz}$	50	$\text{fA}/\sqrt{\text{Hz}}$
-------	-----------------------	---------------------	----	------------------------------

We find $\text{current_noise_input_filter}=1.25\text{pA}$

Bring back at the input in Coulombs by dividing these value by the charge amplifier gain (30dB) : $\text{IRN_filter}=5.91 \text{ nC}$


Then we compute the value flicker noise constant for the voltage noise of the charge amplifier from the datasheet (neglect the thermal one car small in our band)

We find $K_{fa}=1.99 \cdot 10^{-14} \text{ V}^2$

For the current in the band of interest, we have $I^2_{\text{charge amplifier}}=5.06 \cdot 10^{-29} \text{ A}^2$

For the given formula, we got an $\text{IRN_amplifier}=6.04 \cdot 10^{-12} \text{ V}^2$, and so $2.45 \text{ }\mu\text{C}$

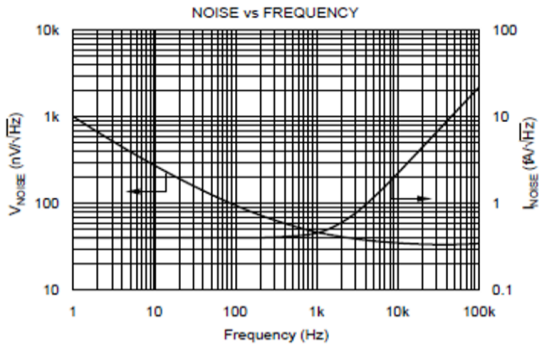The total IRN is so $2.455 \text{ }\mu\text{C}$



Whole chain noise analysis (2/2)



Give the equivalent charge noise of each block of the chain and evaluate their impact.

See previous slide (no impact of the filter)